



Introduction to Verilog

Chien-Ming Wu

TSRI, NARL, Taiwan, R.O.C.

Lan-Da Van

Department of Computer Science

National Yang Ming Chiao Tung University


Taiwan, R.O.C.

Fall, 2023






設計流程 (Design Flow)

Mat 2

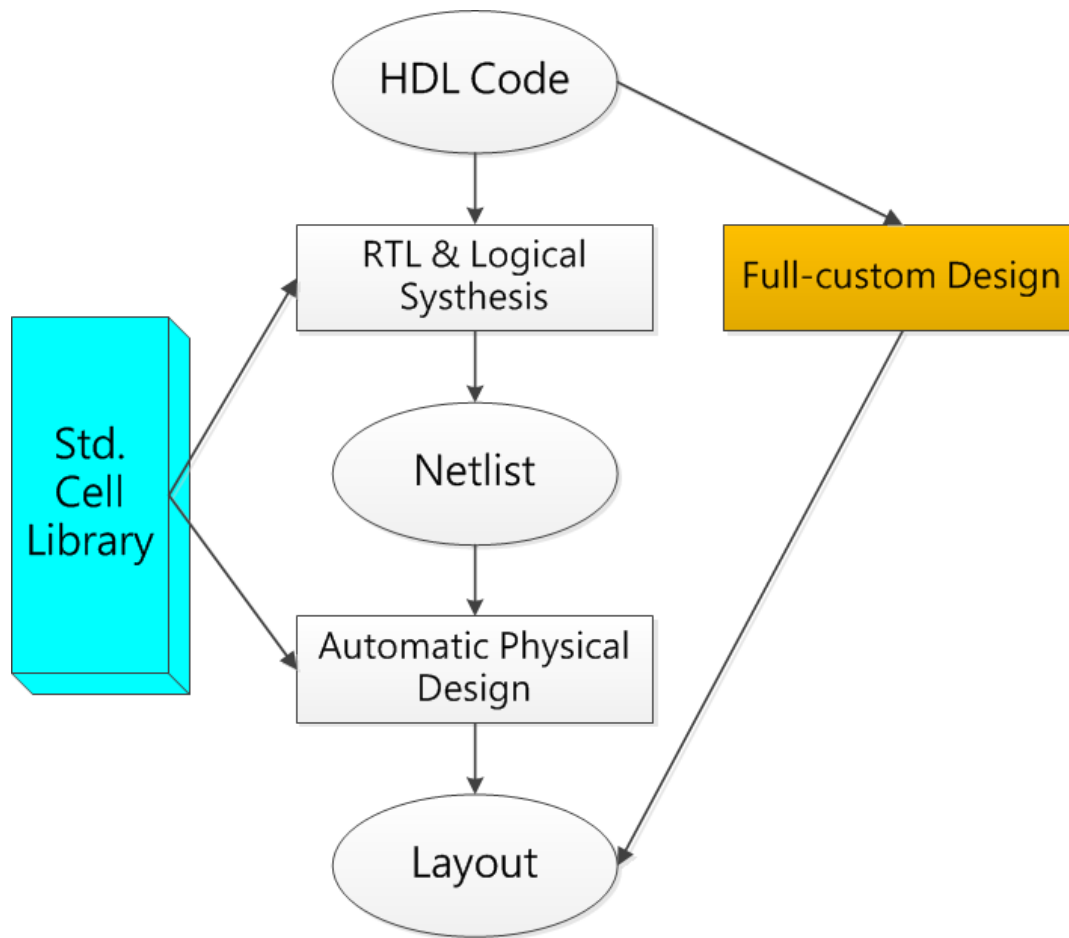
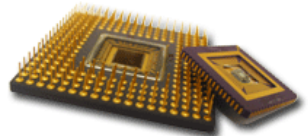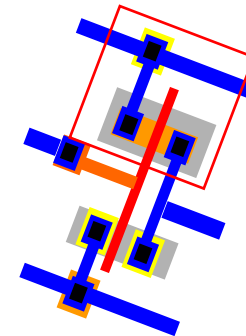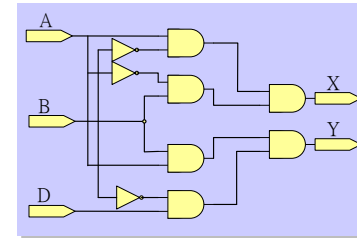
```
always @(posedge clk) begin
  if (sel1) begin
    if (sel2)
      out=in1;
    else
      out=in2;
  end
end
```








Verilog History (from Wikipedia)

Mat 2

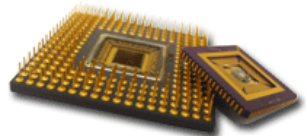- ◆ Verilog HDL是一種硬體描述語言(hardware description language)，為了製作數位電路而用來描述ASICs和FPGA的設計之用。
- ◆ 1995年，Verilog被提交到IEEE併成為**IEEE 1364-1995**標準。我們通常稱這一標準為**Verilog-95**。
- ◆ 2001年，提交了一個改善Verilog-95標準缺陷的新的標準。這一擴展版本成為了**IEEE1364-2001**標準，也就是**Verilog-2001**。



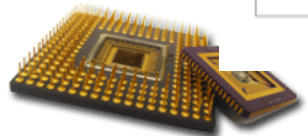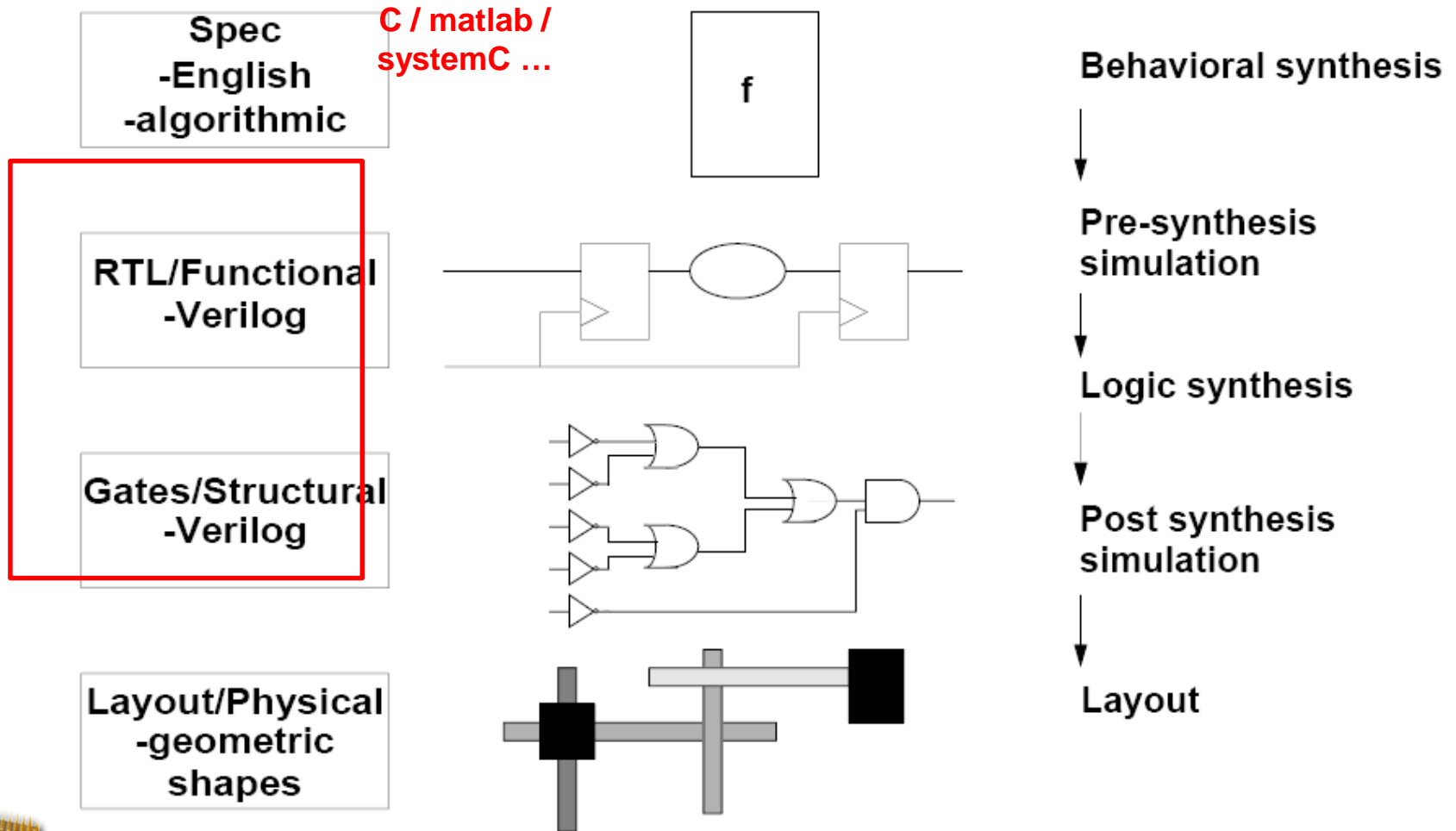



Gate (Structural)

Mat 2

- ◆ The structural level in Verilog is appropriate for small components such as ASIC and FPGA cells.
 - Verilog has built-in primitives, such as the AND gate, that describe basic logic functions. (用內建的邏輯閘(**and, or ...**)描述電路)
 - You can describe your own User Defined Primitives (UDPs).
 - The resulting netlist from synthesis is often purely structural, but you can also use structural modeling for glue logic.
- ◆ The function of the following structural model is represented in Verilog primitives, or gates. It also contains propagation delays:


```

module twomux (out, a,b,s1);

input a,b,s1;
output out;

not u1 (ns1, s1 );
and #1 u2 (sela, a, ns1);
and #1 u3 (selb, b, s1);
or #2 u4 (out, sela, selb);

endmodule
  
```

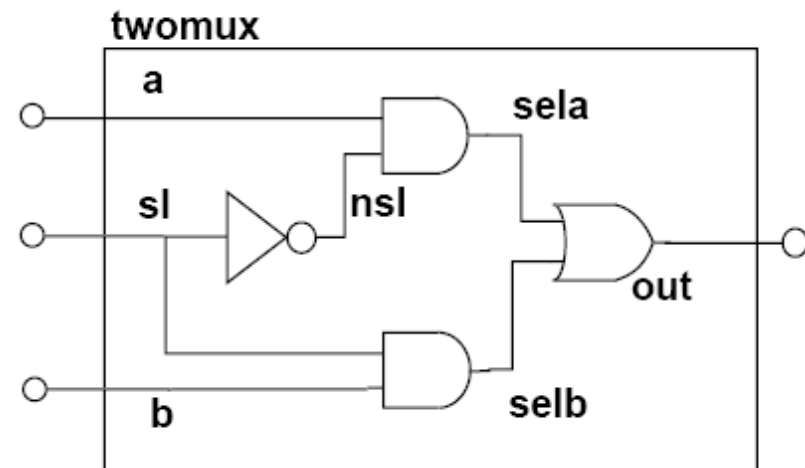



Dataflow




Mat 2

◆ Describe the algorithm in terms of logical data flow. (描述電路中暫存器值資料流動方式)

```

module mux2_1 (out, a, b, sel);
output out;
input a, b, sel;
    assign out = (a&~sel) | (b&sel);
    // or assign out = (sel == 0) ? a :
endmodule

```

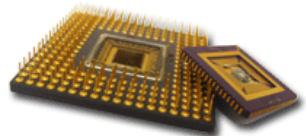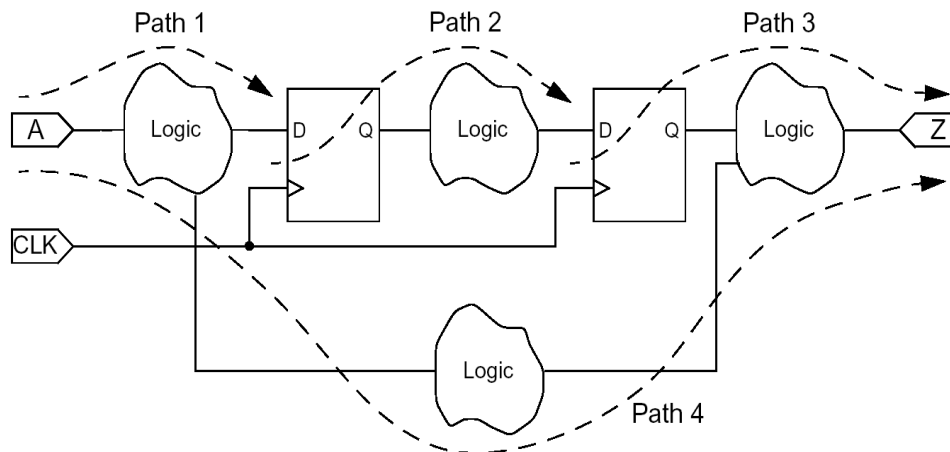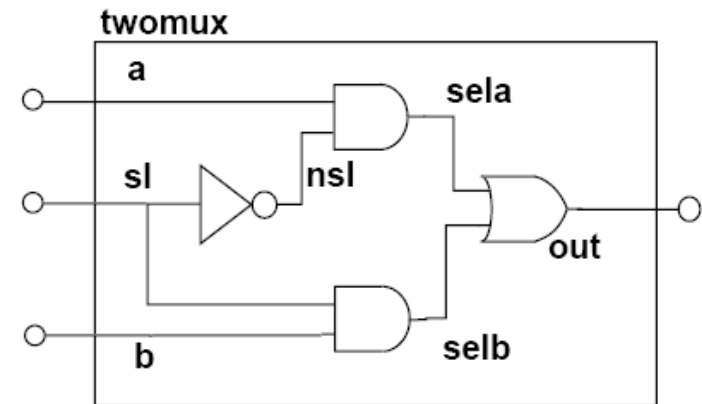




Behavioral


Mat 2

- ◆ Describe the algorithm without concern for the actual logic required to implement it.
- ◆ The behavior of the following MUX is : always, at any change in signals **a** or **b** or **sl**, if **sl** is 0 pass the value of **a** to **out**, else pass the value of **b** to **out**.
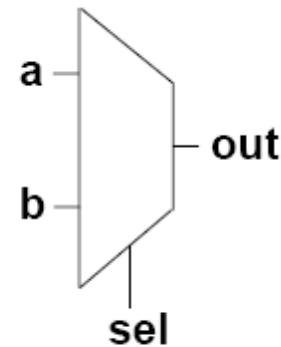
```
module muxtwo (out, a, b, sl);  
  input a,b,sl;  
  output out; reg out;  
  always @(sl or a or b)  
    if (!sl)  
      out = a;  
    else  
      out = b;  
endmodule
```



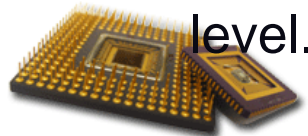- ◆ In a behavioral model, the function of the logic is modeled using high level language constructs, such as **@**, **while**, **wait**, **if** and **case**.
- ◆ Test benches, or test fixtures, are typically modeled at the behavioral level. All behavioral constructs are legal for test benches.





DataFlow/Behavioral/Structural

Mat 2

Data Flow Modeling

```
module DF_AND (in1 , in2 , Out)
```

```
input in1, in2 ;
```

```
output Out ;
```

```
wrie Out ;
```

```
assign Out = in1 & in2 ;
```

```
and a1(Out, in1, in2);
```

```
endmodule
```

Gate/structural Modeling

Behavioral Modeling

```
module Beh_AND (in1 , in2 , Out)
```

```
input in1 , in2 ;
```

```
output Out ;
```

```
reg Out ;
```


```
always @ (in1 or in2)
```

```
begin
```

```
    Out = in1 & in2
```

```
end
```

```
endmodule
```

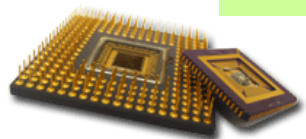



Lexical Conventions in Verilog




Key Language Features:

Verilog Module (1/2)

Mat 2

(1) Verilog Module

◆ 模組(module)是組成一個電路的基本單位

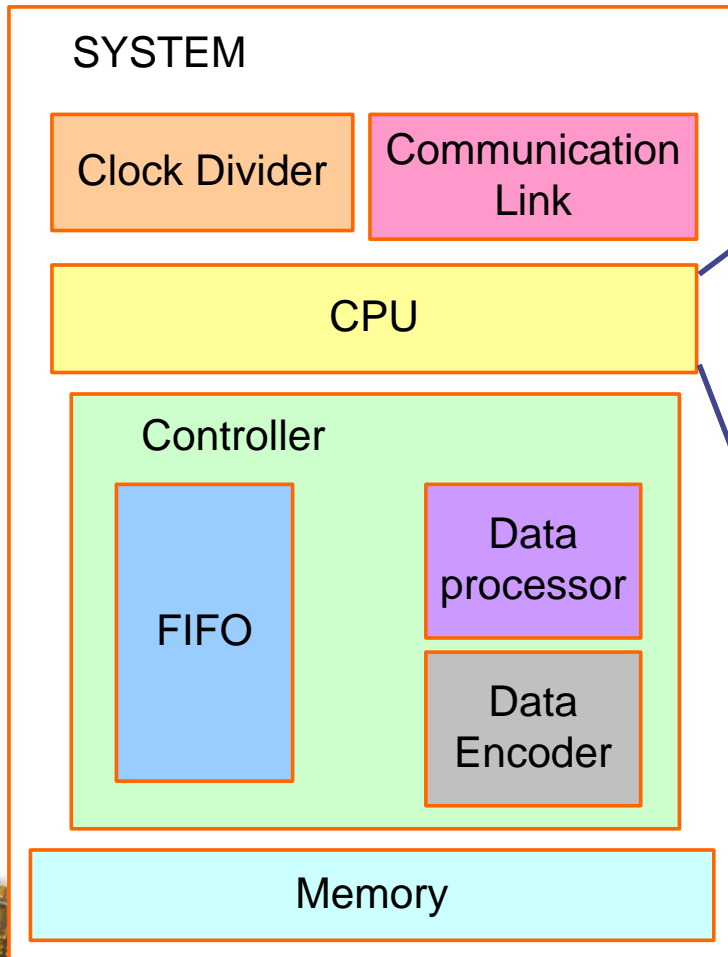

```
module module_name( port_list );
```

port declaration

data type declaration

functionality or structure

task & function declaration

```
endmodule
```



Key Language Features:

Verilog Module (2/2)



Mat 2

(1) Verilog Module

- ◆ Modules are the **basic** building blocks in the design hierarchy.
- ◆ You place the descriptions of the logic being modeled **inside** modules.
- ◆ Modules can represent:
 - A physical block such as an IC or ASIC cell
 - A logical block such as the ALU portion of a CPU design
 - The complete system
- ◆ Every module description **starts** with the keyword **module**, **has a name** (SN74LS74, DFF, ALU, etc.), and **ends** with the keyword **endmodule**
- ◆ Modules define a new scope (level of hierarchy) in Verilog.
- ◆ Example is shown as below :

```
module ALU
.....
.....
endmodule
```

} Logic description(abstraction level)

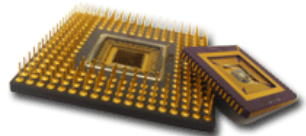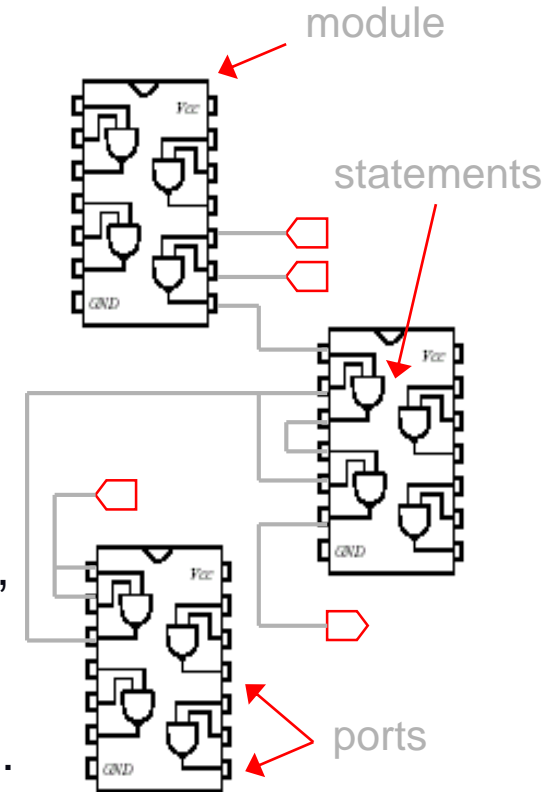




Key Language Features:

Module Ports


Mat 2

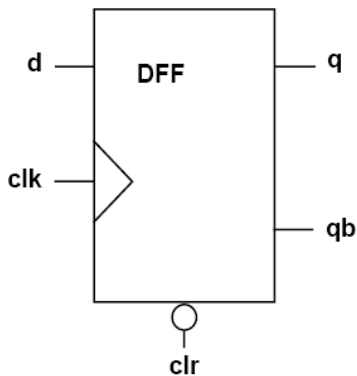(2) Module Ports

- ◆ Modules communicate with the outside world through ports.
- ◆ Module ports are equivalent to the pins in hardware.
- ◆ You list a module's ports in parentheses “()” after the module name.
- ◆ You declare ports to be *input*, *output*, or *inout* (bidirectional) in the module description.
- ◆ DFF Example:



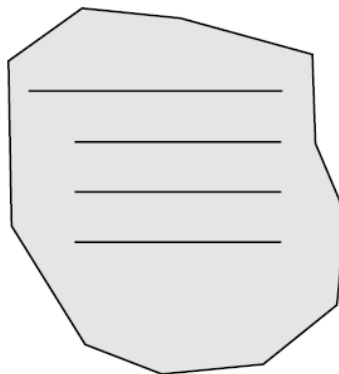
```
module DFF (d, clk, clr, q, qb);  
  input d, clk, clr;  
  output q, qb;
```



```
endmodule
```

input [3:0] c, d;

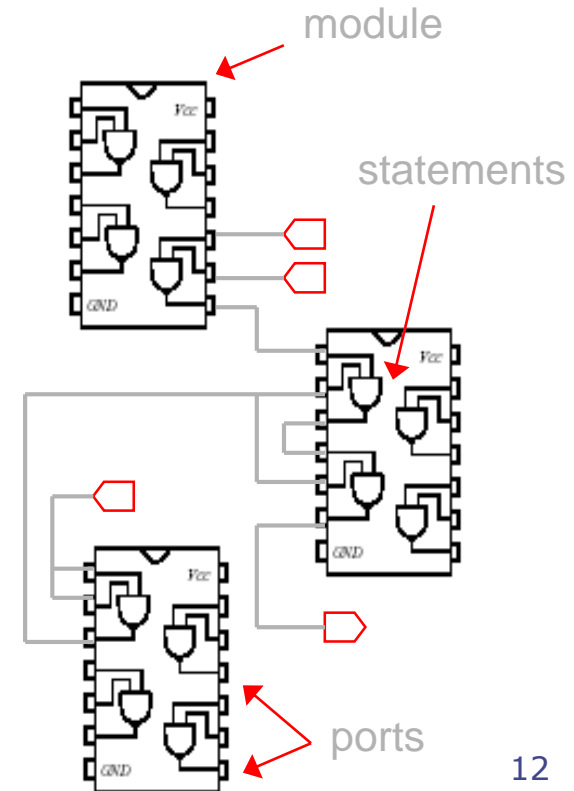




4-Value Logic System in Verilog

Mat 2

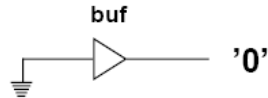
- ◆ The Verilog HDL value set consists of four basic values :




Zero, Low, False, Logic Low, Ground, VSS, Negative Assertion



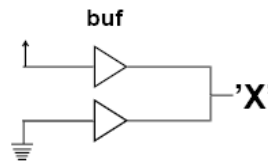One, High, True, Logic High, Power, VDD, VCC, Positive Assertion




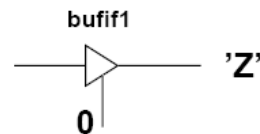X, Unknown: Occurs at Logical Conflict Which Cannot be Resolved



HiZ, High Impedance, Tri-States, Disabled Driver (Unknown)

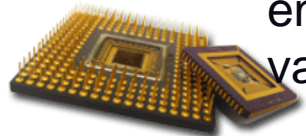- ◆ The “unknown” logic value in Verilog is **not** the same as “don't care”. It represents a situation where the value of a node cannot be predicted. In real hardware, this node will most be at either 1 or 0.
- ◆ When the Z value is present at the input of a gate, or when it is encountered in an expression, the effect is usually the same as an x value.






Integer Constants

Mat 2

In Verilog, **constant** values (literals) can be integers or reals.

- ◆ **Integers** can be sized or unsized. Sized integers are represented as **<size>'<base><value>**
 - <size> is the size in bits.
 - <base> can be b(binary), o(octal), d(decimal), or h(hexadecimal).
 - <value> is any legal number in the selected base, **including x and z bits**.
- ◆ Underscores(_) in number are ignored (4'b10_11 = 4'b1011)
 - Underscores(_) can be put anywhere in a constant number, except the beginning, to improve readability.
- ◆ Unsized integers default to 32bits (Ex: c='ha5; This is a 32bits hexadecimal, c=a5)
- ◆ The base default to decimal
- ◆ The base and value fields are **case insensitive** (Ex: Decimal (d or D都可以))
- ◆ Example:
 - **8'b1001_0011** is a 8-bits binary number
 - **3'B01x** is a 3-bits binary number with the LSB unknown
 - **659** is a decimal number
 - **'h837FF** is a hexadecimal number

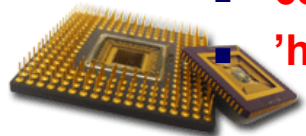



Identifiers

Mat 2

- ◆ An identifier is used to given an object, such as a register or a module a **name** so that it can be referenced from other places in a description.
- ◆ An identifier shall be any sequence of letters (a-z, A-Z), digits (0-9), dollar signs '\$', and underscore characters '_'.
 - ◆ The first character of an identifier shall be a letter or an underscore character.
 - ◆ The first character must **not** be a digit or \$
 - ◆ Identifiers can be up to 1023 characters long.
 - ◆ Names of modules, ports, and instances are identifiers.


```

module MUX2_1 (out, a, b, sel);
  output out;
  input a, b, sel;
  not not1 (sel_, sel);
  and and1 (a1, a, sel_);
  and and2 (b1, b, sel);
  or or1 (out, a1, b1);
endmodule
  
```

Verilog Identifiers

Example of illegal identifiers :

- 34net
- a*b_net
- n@238

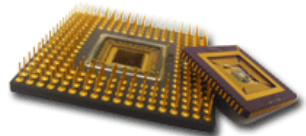




Special Language Tokens: \$

Mat 2

System Tasks and Functions

\$<identifier>

- ◆ The '\$' sign denotes Verilog system **tasks** and **functions**.
 - ◆ A number of system tasks and functions are available to perform different operations, such as:
 - Finding the current simulation time (\$time))
 - Displaying/monitoring the values of the signal (\$display, \$monitor)
 - Stopping the simulation (\$stop)
 - Finishing the simulation (\$finish)
- \$monitor (\$time, "a = %b, b = %h", a, b);

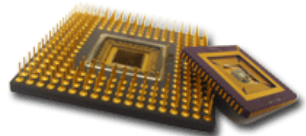




Special Language Tokens:

Mat 2

Delay Specification

- ◆ The pound sign (#) character denotes the **delay** specification for procedural statements, and for gate instances but not module instances.
- ◆ The # delay for gate instances is referred to by many names, including gate delay, propagation delay, intrinsic delay, and intra-object delay.
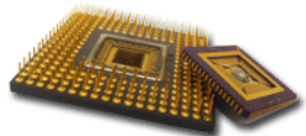
```
module MUX2_1 (out, a, b, sel) ;  
  output out ;  
  input  a, b, sel;  
  not #1 not1(sel_,sel);  
  and #2 and1(a1,a,sel_);  
  and #2 and2(b1,b,sel);  
  or  #1 or1(out,a1,b1);  
endmodule
```





Data Types

Mat 2

◆ Nets

- Represent physical connection between devices (**default = z**)
- Verilog automatically propagates a new value onto a net when the drivers on the net change value. (不斷被驅動 => 改變它的內含值)
- Value is that of its drivers such as a continuous assignment (data flow modeling) or a gate

```
wire [MSB:LSB] DAT; // vector wire
```

```
wire RDY, START;
```

```
wire [2:0] ADDR;
```


◆ Registers

- Represent a variable that can hold a value. (**default = x**). (reg表示資料儲存，除非給定新的數值，否則數值會一直維持。)
- They are used in procedural blocks (behavioral modeling).

```
reg A, B, C; // 1-bit scalars
```

```
reg [0:3] STRANGE;
```

```
reg [0:7] QBUS;
```

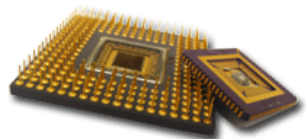



Structural Modeling



Structural Modeling

Mat 2

- ◆ A structural model in Verilog represents a **schematic**.
- ◆ A structural model is created using existing components.
- ◆ When you use components to create another model, you create instances of these components.

```



module MUX4x1(Z, D0, D1, D2, D3, S0, S1)
output Z;
input D0, D1, D2, D3, S0, S1;
and (T0, D0, S0_, S1_),
      (T1, D1, S0_, S1_),
      (T2, D2, S0, S1_),
      (T3, D3, S0, S1);
not (S0_, S0), (S1_, S1);
or (Z, T0, T1, T2, T3);
endmodule

```

```

module rs_latch (y, yb, r, s);
output y, yb;
input r, s;
nor n1(y, r, yb);
nor n2(yb, s, y);
endmodule

```

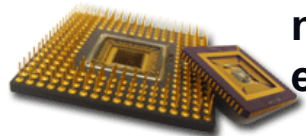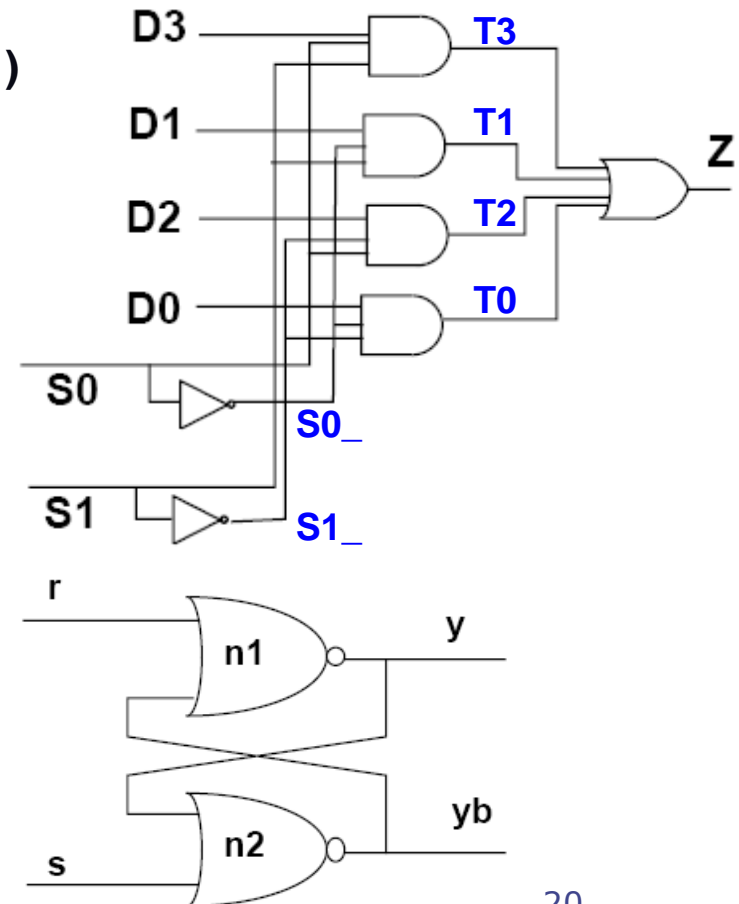




Verilog Expressions and Operators



Verilog Expressions

Mat 2

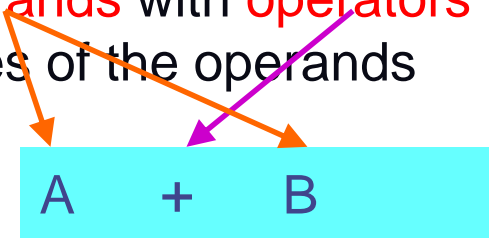
- ◆ An expression is a construct that combines **operands** with **operators** to produce a result that is a function of the values of the operands and the semantic meaning of the operator.



- ◆ An operand can be one of the following :
 - Number (including real)
 - net, net bit-select, net part-select.
 - register, integer, time, register bit-select, register part-select.
 - memory element
 - A call to a user-defined function or system-defined function that returns any of the value.

◆ Example:

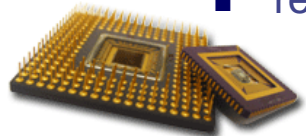- `real a, b, c;`
`c = a + b; // a and b are real operands`
- `reg_out = reg1[3:0] + reg2[3:0] // reg1[3:0], reg2[3:0] are part-select register operands`
- `ret_value = calculate_parity (A, B) // calculate_parity is user-defined function`





Operator Types

Mat 2

- ◆ The following table shows the operators in Verilog, in order of precedence.
- ◆ Note that “and” operators always have higher precedence than “or” operators of the same type.

Type of Operators	Symbols
Concatenate & Replicate (連接運算子)	{ } { { } }
Unary (精簡運算子)	! ~ & ^
Arithmetic (算數運算子)	** * / % + -
Logical shift (位移運算子)	<<< >>> << >>
Relational (關係運算子)	> < >= <=
Equality (等於運算子)	== === != !==
Binary bit-wise (位元邏輯運算子)	& ^ ~^
Binary logical (邏輯運算子)	&&
Conditional (條件運算子)	? :

Highest
↑
Precedence
↓
Lowest

`a < b-1 && c != d || e == f` → worse
`(a < b-1) && (c != d) || (e == f)` → better




Concatenation and Replication Operators

Mat 2

◆ { } concatenation


Ex. $a = \{b, c\};$

MSB LSB

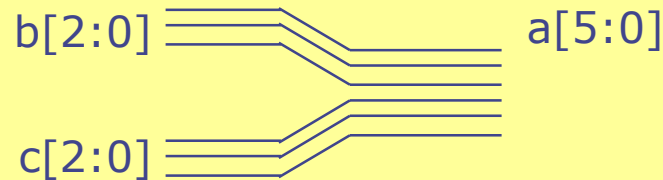

◆ {{ }} replication


Ex. $a = \{2\{c\}\};$

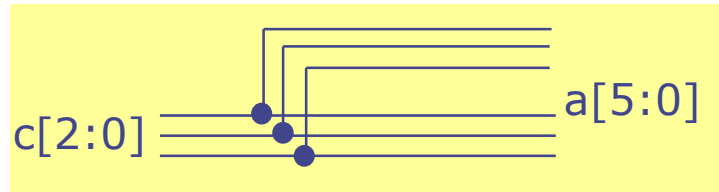

$a[4:0] = \{b[3:0], 1'b0\}; \quad a = b \ll 1;$

$\{a, b[3:0], c, 2'b01\} = \{a, b[3], b[2], b[1], b[0], c, 1'b0, 1'b1\}$

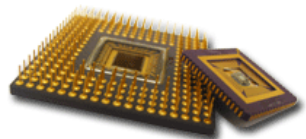$\{a, \{3\{a, b\}\}, b\} = \{a, a, b, a, b, a, b, b\}$





Unary Reduction Operators

Mat 2


&	and
	or
^	xor
~^	xnor
^~	xnor

- ◆ Reduction operators perform a bit-wise operation on all the bits of a **single operand**.
- ◆ The result is always 1'b1, 1'b0 or 1'bx.

```

module reduction();
reg val;
reg [3:0] rega, regb;
initial begin
    rega = 4'b0100;
    regb = 4'b1111;
end
initial fork
    #10 val = &rega ;           // val = 0
    #20 val = |rega ;           // val = 1
    #30 val = &regb ;           // val = 1
    #40 val = |regb ;           // val = 1
    #50 val = ^rega ;           // val = 1
    #60 val = ^regb ;           // val = 0
    #70 val = ~|rega;           // (nor) val = 0
    #80 val = ~&rega;           // (nand) val = 1
    #90 val = ^rega && &regb;    // val = 1
    #99 $finish;
join
endmodule

```

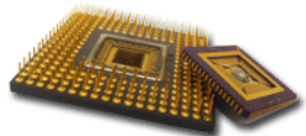



Arithmetic Operators

Mat 2


- +** add
- subtract
- *** multiply
- /** divide
- %** modulus
- **** exponent (power) (verilog-2001)

- ◆ An assignment of a **negative** result to a reg or other unsigned variable uses the **2's complement**.
- ◆ If any bit of any operand is **unknown(x)** or **tristate(z)**, the result is simply **unknown(x)**.
- ◆ In integer division, the remainder is discarded.

```

module arithops ( );
integer ans, int;
parameter five = 5;
reg [3:0] rega, regb;
reg [3:0] num;
initial begin
    rega = 3;
    regb = 4'b1010;
    int = -3;
end
initial fork
    #10 ans = five * int;           // ans = -15
    #20 ans = (int + 5)/2;         // ans = 1
    #30 ans = five/int;           // ans = -1
    #40 num = rega + regb;         // num = 1101
    #50 num = rega + 1;           // num = 0100
    #60 num = int;                // num = 1101
                                   (2補數)
    #70 num = regb % rega;         // num = 1
    #80 ans = 2**3                 // ans = 8
    #90 $finish;
join
endmodule

```

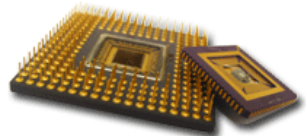



Shift Operators

>> **shift right**

<< **shift left**

>>> **arithmetic shift right** (verilog-2001)

<<< **arithmetic shift left** (verilog-2001)

◆ a << n

- a shift left n bits, and fills in **zero** bits

◆ b >> n

- b shift right n bits, and fills in **zero** bits

◆ c <<< n

- c shift left n bits, and fills in **zero** bits

◆ d >>> n

- d shift right n bits, and fills in **signed** bits

◆ Shift operators perform left or right bit shifts to the **first operand**.

◆ The second operand is treated as **unsigned**.

◆ If the second operand has unknown or tristate bits, the result is **unknown**.

```
module shift ();
reg [5:0] numa, numb, numc, numd, nume;
reg [3:0] rega;
reg signed [3:0] regb;
initial begin
    rega = 4'b1011;
    regb = 4'b1101;
end
initial begin
    #10 numa = rega << 2 ; // rega =    1 0 1 1
                           // numa= 1 0 1 1 0 0

    #20 numb = rega >> 3;  // rega =    1 0 1 1
                           // numb= 0 0 0 0 0 1

    #30 numc = regb <<< 1; // regb =    1 1 0 1
                           // numc= 1 1 1 0 1 0

    #40 numd = regb >>> 2; // regb =    1 1 0 1
                           // numd= 1 1 1 1 1 1

    #50 nume = regb >> 2;  // regb =    1 1 0 1
                           // nume= 0 0 1 1 1 1

    #300 $finish;
end
endmodule
```



Relational Operators

Mat 2

- > greater than
- < less than
- >= greater than or equal
- <= less than or equal


- ◆ The result is always 1'b1, 1'b0 or 1'bx.
- ◆ **Note:** relational operations have **lower** precedence than arithmetic operations.

$a < \text{size} - 1$
 $a < (\text{size} - 1)$

} same expression

$\text{size} - (1 < a)$
 $\text{size} - 1 < a$

} different expression

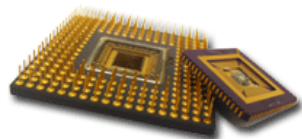

```

module relationals ();
reg [3:0] rega, regb, regc;
reg val;
initial begin
    rega = 4'b0011; // 3
    regb = 4'b1010; // 10
    regc = 4'b0x10;
end
initial fork
    #10 val = regc > rega; // val = x
    #20 val = regb < rega; // val = 0
    #30 val = regb >= rega; // val = 1
    #40 val = regb > regc; // val = 1
    #50 $finish;
join
endmodule
    
```



Equality Operators (1/3)

Mat 2

== **logical equality**
!= **logical inequality**

◆ The result is always 1'b1, 1'b0 or 1'bx

==	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

```
module equalities1();
reg [3:0] rega, regb, regc;
reg val;
```

```
initial begin
```

```
    rega = 4'b0011; // 3
```

```
    regb = 4'b1010; // 10
```

```
    regc = 4'b1x10;
```

```
end
```

```
initial fork
```

```
    #10 val = rega == regb ; // val = 0
```

```
    #20 val = rega != regc;  // val = 1
```


```
    #30 val = regb != regc;  // val = x
```

```
    #40 val = regc == regc;  // val = x
```

```
    #50 $finish;
```

```
join
```

```
endmodule
```

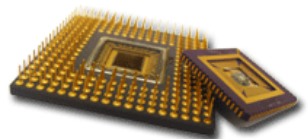



Equality Operators (2/3)

Mat 2


=== **identity (case equality)**
!== **nonidentity (case inequality)**

◆ The result is always 1'b1 or 1'b0

===	0	1	x	z
0	1	0	0	0
1	0	1	0	0
x	0	0	1	0
z	0	0	0	1

```

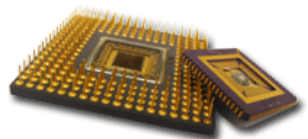module equalities2();
reg [3:0] rega, regb, regc;
reg val;
initial begin
    rega = 4'b0011; // 3
    regb = 4'b1010; // 10
    regc = 4'b1x10;
end
Initial fork
    #10 val = rega === regb; // val = 0
    #20 val = rega !== regc; // val = 1
    #30 val = regb !== regc; // val = 1
    #40 val = regc === regc; // val = 1
    #50 $finish;
join
endmodule
  
```





Equality Operators (3/3)


Mat 2

- ◆ **=** is the **assignment** operator. It copies the value of the RHS of the expression to the LHS.
- ◆ **==** is the **logical equality** operator
 - Which the logical equality operator, an X in either of the operand is logicity unknown.
- ◆ **===** is the **case equality** operator
 - With the case equality operator, the result can still evaluate to true (1) or false (0) when x or z values are present in the operands.

==	0	1	x	z
0	1	0	x	x
1	0	1	x	x
x	x	x	x	x
z	x	x	x	x

===	0	1	x	z
0	1	0	0	0
1	0	1	0	0
x	0	0	1	0
z	0	0	0	1

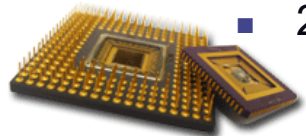- 2'b0x === 2'b1x evaluates to 0, because they are not equal.
- 2'b1x == 2'b1x evaluates to 1'bx, because they may or may not be equal.






Bit-Wise Operators

Mat 2

~ not
 & and
 | or
 ^ xor
 ~^ xnor
 ^~ xnor

- ◆ Bit-wise binary operators perform **bit-wise manipulations on two operands**. They compare each bit in one operand with its corresponding bit in the other operand to calculate each bit for the result.
- ◆ Because you can declare the operands to be of different sizes, the **smaller** operand is **zero-extended** to the size of the larger operand during the operation.

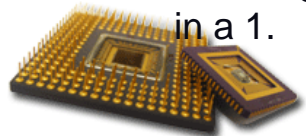Note: Unknown bits in an operand do not necessarily lead to unknown bits in the result. For example, at time 50 above, the unknown bit in **regc** is ORed with a 1 in **regb**, resulting in a 1.



```

module bitwise ();
reg [3:0] rega, regb, regc;
reg [3:0] num;

```

```

initial begin

```

```

    rega = 4'b1001;
    regb = 4'b1010;
    regc = 4'b11x0;

```

```

end

```

```

initial fork

```

```

#10 num = rega & 0;      // num = 0000
#20 num = rega & regb;   // num = 1000
#30 num = rega | regb;   // num = 1011
#40 num = regb & regc;   // num = 10x0
#50 num = regb | regc;   // num = 1110
#60 $finish;

```

```

join

```

```

endmodule

```




Logical Operators (Binary)

Mat 2


!	not
&&	and
	or

- ◆ The result of a logical operation is always 1'b0, 1'b1 or 1'bx.
- ◆ Logical **binary** operators operate on logic values. If an operand contains all zeroes, it is **false** (logic 0). If it contains any ones, it is **true** (logic 1). If it is **unknown** (contains only zeroes and/or unknown bits), its logical value is **ambiguous**.
- ◆ The logical negation operator reduces an operand to its logical inverse. For example, if an operand contains all zeroes, it is false (logic 0), so its inverse is true (logic 1).

```
module logical ();
parameter five = 5;
reg ans;
reg [3:0] rega, regb, regc;
```

```
Initial begin
    rega = 4'b0011;
    regb = 4'b10xz;
    regc = 4'b0z0x;
end
```

```
initial fork
    #10 ans = rega && 0;      // ans = 0
    #20 ans = rega || 0;     // ans = 1
    #30 ans = rega && five;   // ans = 1
    #40 ans = regb && rega;   // ans = 1
    #50 ans = regc || 0;     // ans = X
    #60 $finish;
join
endmodule
```

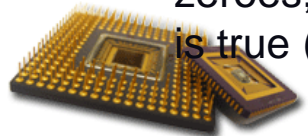




Note

Mat 2

$a = 1011$
 $b = 0010$

bit-wise	unary reduction	logical
$a \mid b = 1011$	$ a = 1$	$a \parallel b = 1$
$a \& b = 0010$	$\& a = 0$	$a \&\& b = 1$

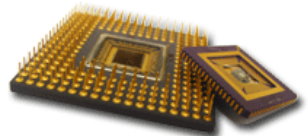



Logical Versus Bit-Wise Negation

Mat 2

! **logical (not)**
 ~ **bit-wise (not)**

- ◆ The logical negation will return 1'b0, 1'b1, or 1'bx.
- ◆ Bit-wise negation returns a value with the same number of bits that are in the operand.

```
module negation();
reg [3:0] rega, regb;
reg [3:0] bit;
reg log;
```

```
initial begin
```

```
    rega = 4'b1011;
```

```
    regb = 4'b0000;
```

```
end
```

```
initial fork
```

```
    #10 bit = ~rega;    // num = 0100
```

```
    #20 bit = ~regb;    // num = 1111
```


```
    #30 log = !rega;    // num = 0
```

```
    #40 log = !regb;    // num = 1
```

```
    #50 $finish;
```

```
join
```

```
endmodule
```

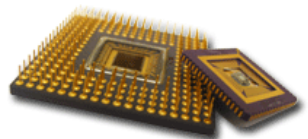




Conditional Operator (1/2)

Mat 2

- ◆ The syntax for the conditional operator is :
 - $\text{<LHS> = <condition> ? <true_expression> : <false_expression>;$
- ◆ This can be read as :
 - If condition is TRUE,
then LHS = true_expression, else LHS = false_expression.
- ◆ If the condition is unknown, and the true_expression and false_expression are not equal, the output is unknown.
 - if sel is 0 then out is set equal to a,
if sel is 1 then out is set equal to b,
if sel is unknown, a is 0, and b is 0, then out is set equal to 0,
if sel is unknown, a is 0, and b is 1, then out is unknown.

assign out = (sel == 0) ? a : b;

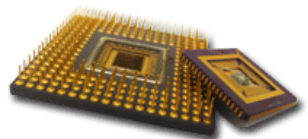





Conditional Operator (2/2)

Mat 2


? : conditional

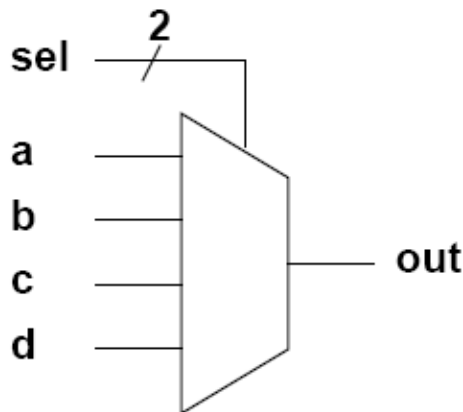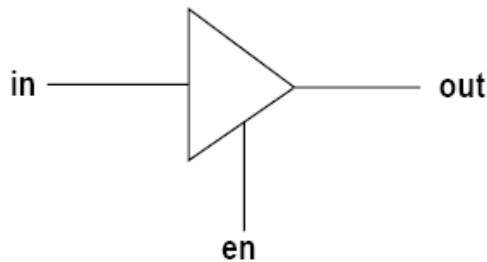- ◆ An unknown value on the condition will result in an unknown value on out.



```
module likebufif (in,en,out);
input in;
input en;
output out;
    assign out = (en == 1) ? in : 'bz;
endmodule
```
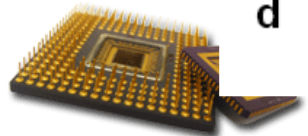
```
module like4to1 (a,b,c,d,sel,out);
input a,b,c,d;
input [1:0] sel;
output out;
    assign out = (sel == 2'b00) ? a :
                  (sel == 2'b01) ? b :
                  (sel == 2'b10) ? c : d;
endmodule
```






Dataflow Modeling




A Full Adder Example

Mat 2
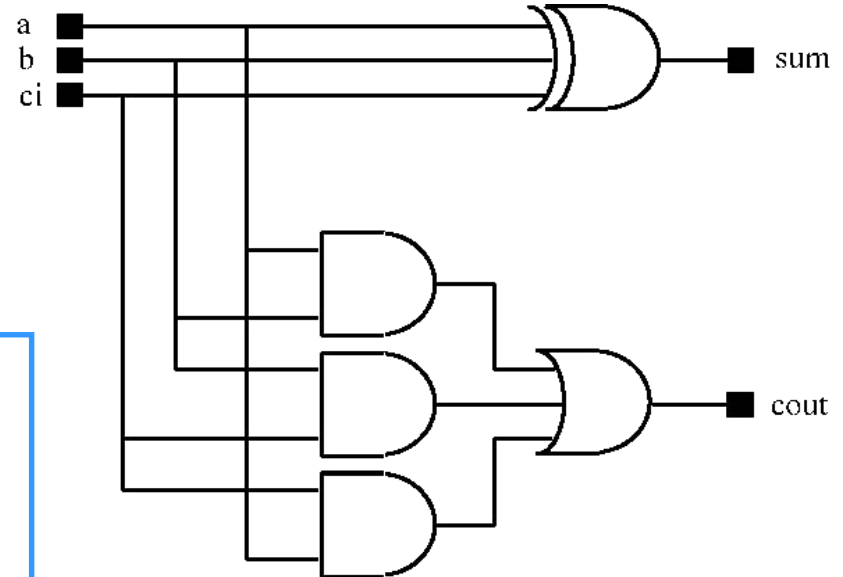
```
module fadder (sum,cout,a,b,ci);  
  //port declaration  
  output sum, cout;  
  input  a, b, ci;  
  
  //netlist declaration  
  xor u0 (sum, a, b, ci);  
  and u1 (net1, a, b);  
  and u2 (net2, b, ci);  
  and u3 (net3, ci, a);  
  or  u4 (cout, net1, net2, net3);  
endmodule
```



`assign {cout, sum} = a + b + ci;`

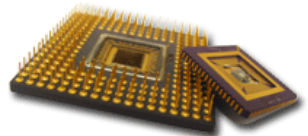




Continuous Assignments (1/4)

Mat 2

- ◆ You can model combinational logic with **continuous assignments**, instead of using gates and interconnect nets.
- ◆ Use continuous assignments outside of a procedural block.
- ◆ Use a continuous assignment to drive a value onto a net.
- ◆ The LHS is updated at any change in the RHS expression, after a specified delay.
 - Continuous assignments can **only contain simple, left-hand side delay** (i.e. limited to a **# delay**), but because of their continuous nature, @ timing control is unnecessary.
- ◆ Syntax for an explicit continuous assignment:
 - **<assign>** [#delay] [strength] <net_name> = <expression>
 - **<assign>** [#delay] [strength] <net1_name> = <exp1>
 [#delay] [strength] <net2_name> = <exp2>
 ...
 [#delay] [strength] <netn_name> = <expn>

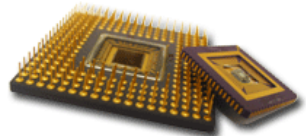




Continuous Assignments (2/4)

Mat 2

- ◆ The assignment is **always active** (continuous assignment)
 - Whenever any change on the RHS of the assignment occurs, it is evaluated and assigned to the LHS.
- ◆ You can make continuous assignments explicit or implicit:

wire [3:0] a;	
assign a = b + c; // explicit	wire [3:0] a = b + c; // implicit
- ◆ It's not allowed which required a concatenation on the LHS.

wire [7:0] {co, sum} = a + b + ci;	→ Error !!
assign {co, sum} = a + b + ci;	→ OK !!
- ◆ **<assign> [#delay] [strength] <net_name> = <expression>**
 - ◆ wire [7:0] (**strong1, weak0**) **#(3,5,2)** o1 = in; // strength and delays

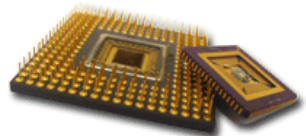



Continuous Assignments (3/4)

Mat 2

```


module assigns (o1, o2, eq, AND, OR, even, odd, one, SUM, COUT, a, b, in, sel, A, B, CIN);
output [7:0] o1, o2;
output [31:0] SUM;
output eq, AND, OR, even, odd, one, COUT;
input a, b, CIN;
input [1:0]sel;
input [7:0] in;
input [31:0] A, B;
    wire [7:0] #3 o2;                                // No assignment yet, but a delay
    tri AND = a&b, OR = a|b;                          // two assignments
    wire #10 eq = (a == b);                          // implicit, with delay
    wire [7:0] (strong1, weak0) #(3,5,2) o1 = in;     // strength and delays

    assign o2 [7:4] = in [3:0], o2 [3:0] = in [7:4];  // part-select

    tri #5 even = ^in, odd = ~^in;                   // delay, two assignments

    wire one = 1'b1;                                // Constant assignment
    assign {COUT, SUM} = A + B + CIN ;              // Assignment to a concatenation
endmodule

```

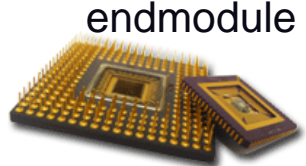



Continuous Assignments (4/4)

Mat 2


<assign> [#delay] [strength] <net_name> = <expression>

◆ LHS (left hand side)

- To any **net** type
- To bit- or part-selects of vectored nets // assign o2 [7:4] = 4'hc;
- To several nets at once in a concatenation // assign {COUT, SUM} = A + B + CIN ;

◆ RHS (right hand side)

- From any expression (**composed of nets or registers or both**), including a constant // assign w = ({a, b} & c) | r ; assign w = 1'b1;
- With a propagation delay and strengths // wire [7:0] (strong1, weak0) #(3,5,2) o1 = in
- From the return values of user-defined functions // assign w = f(...)

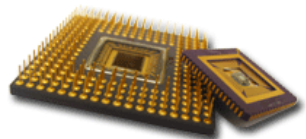




Behavioral Modeling



Behavioral Modeling

Mat 2

- ◆ Behavioral modeling enables you to describe the system at a **high level** of abstraction.
 - At this level of abstraction, implementation is not as important as the overall functionality of the system. **(ps. 並不是Behavioral Modeling就不能合成)**
- ◆ High-level programming language constructs are available in Verilog for behavioral modeling.
 - These include ***wait***, ***while***, ***if then***, ***case***, and ***forever***.
- ◆ Behavioral modeling in Verilog is described by specifying a set of **concurrently active procedural blocks** that together describe the operation of the system.

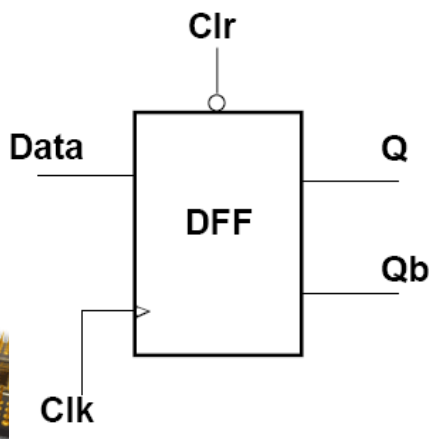

DFF



At every positive edge of Clk
If Clr is not low
Set Q to the value of Data
Set Qb to inverse of Data

Whenever Clr goes low
Set Q to 0
Set Qb to 1

```
always @(posedge clk)
begin
  if (clr == 0)
  begin
    q <= 1'b0;
    qb <= 1'b1;
  end
else
  begin
    q <= d;
    qb <= ~d;
  end
end
```

Mat 2



- # Timing controls

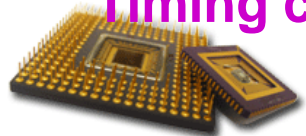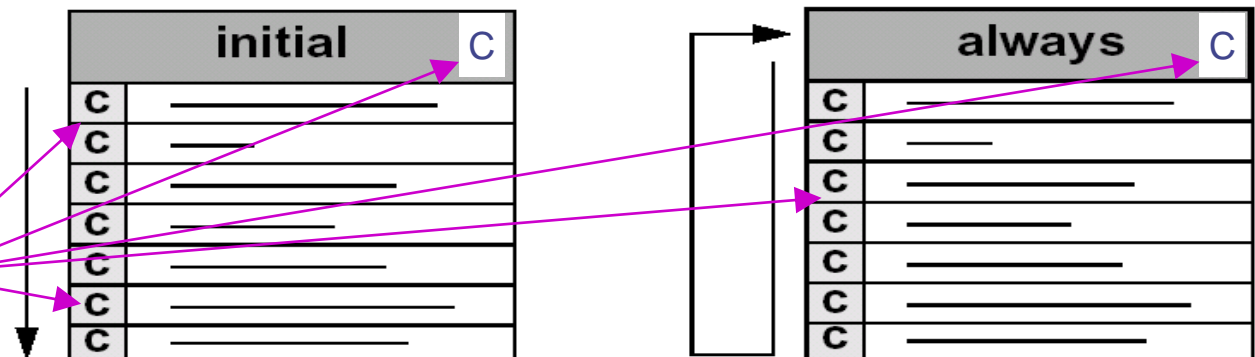



Example of *initial* Statements



Mat 2

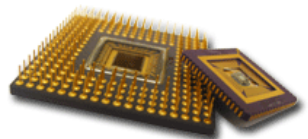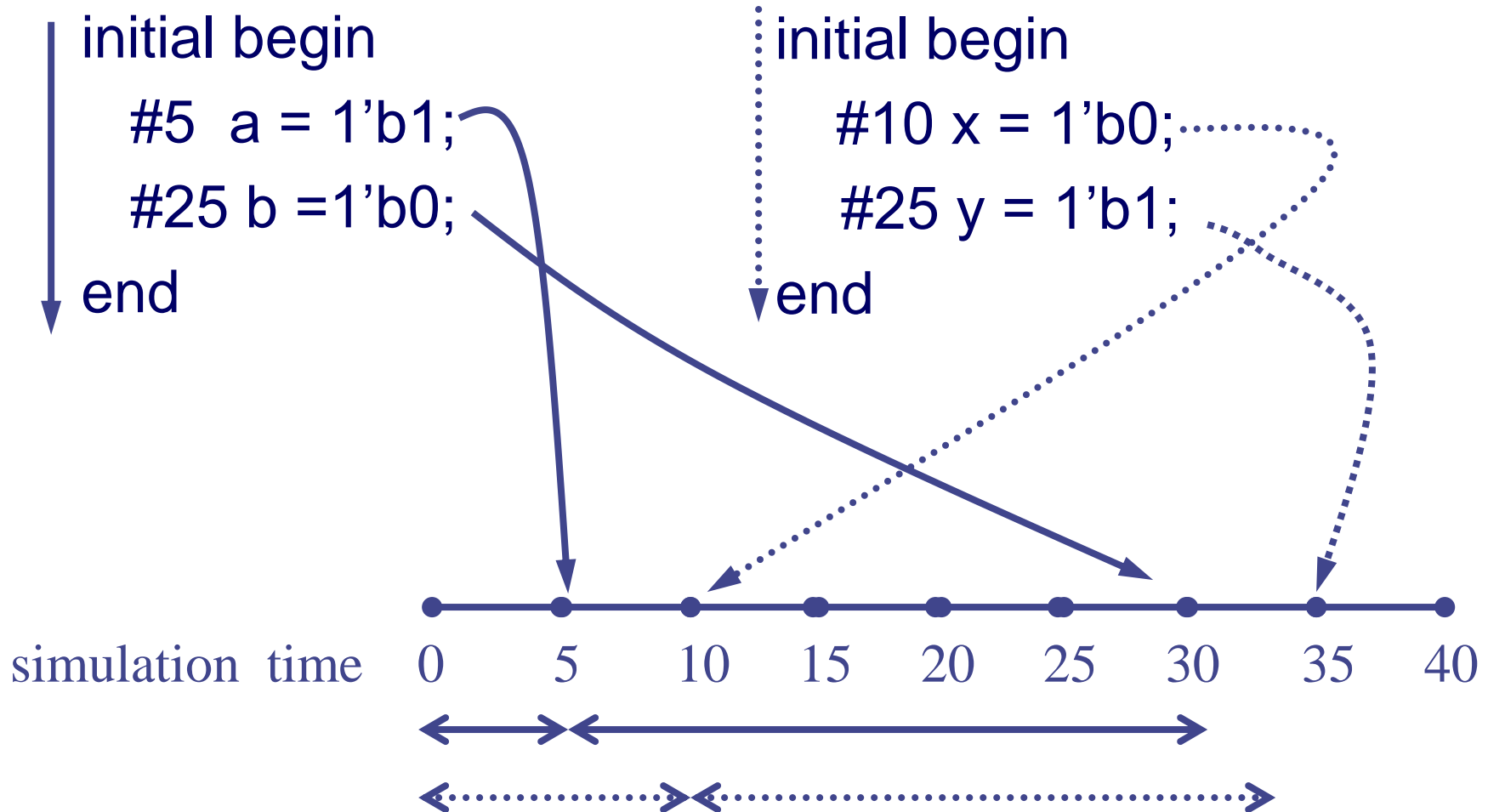



Example of *always* Statements

Mat 2

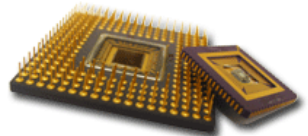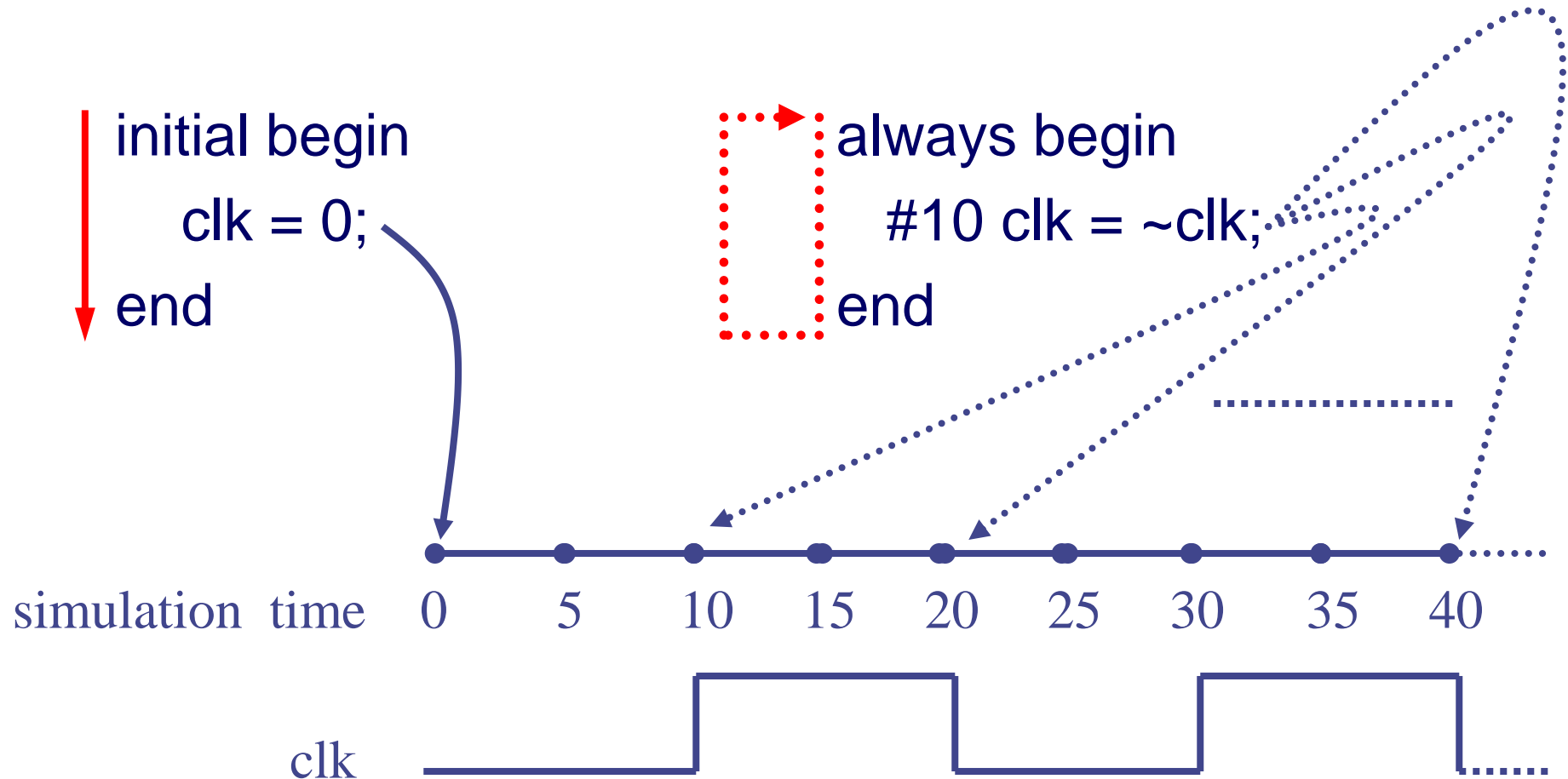








Block Statements

Mat 2

Block statements are used to **group two or more statements together**.

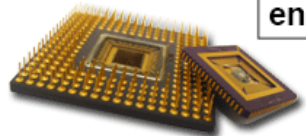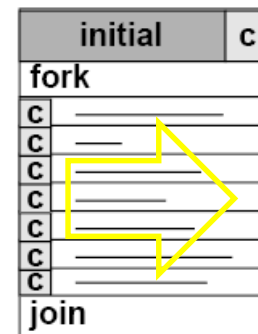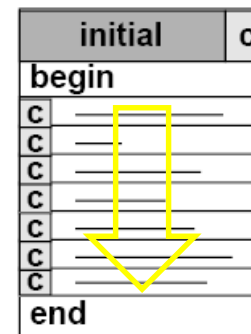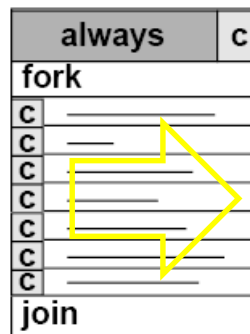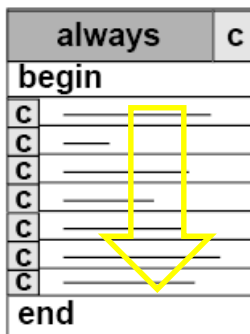- ◆ **Sequential** block statements are enclosed between the key words ***begin*** and ***end***.
- ◆ **Parallel** block (**concurrent** block) statements are enclosed between the key words ***fork*** and ***join***.
 - Note that ***fork-join*** blocks are typically **not synthesizable** and result in inconsistent synthesis result, it is also handled **inefficiently** by some simulators.





Block Statements: *Examples*


Mat 2

- ◆ In a **sequential** block, statements are evaluated and executed **one** after the other.

begin

```
#5 a = 3; // #5
#5 a = 5; // #10
#5 a = 4; // #15
```

end


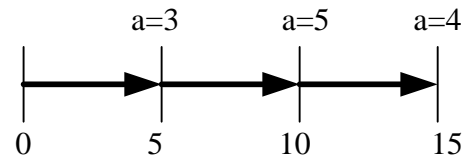


- ◆ In a **concurrent** block, all statements are **immediately scheduled** to be evaluated and executed after their respective delays.

fork

```
#5 a = 3; // #5
#15 a = 5; // #15
#10 a = 4; // #10
```

join

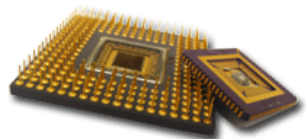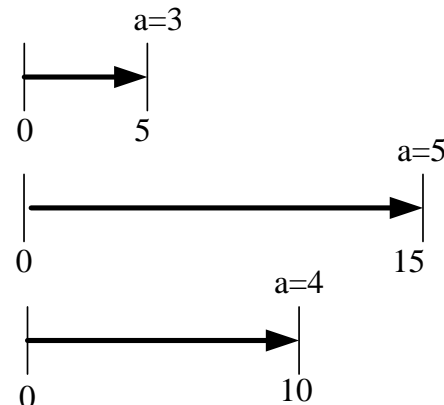



Components in Procedural Blocks

Mat 2

◆ Procedural blocks have the following components:

控制電路何時/
何種條件動作

描述電
路行為

- Timing controls to control the execution of the block and the statements in the block
- Procedural assignment statements to describe the data flow **within the block**
- High-level constructs (loops, conditional statements) to describe the functional operation of the block

Procedural block

```
module add_mul(out, a, b);
input [2:0] a, b;
output [3:0] out;
reg [3:0] out;
```

Timing control


```
always@(a or b)
if (a > b)
out = #5 a + b;
```

```
else
out = #8 a * b;
```

High level
constructs

Procedural
assign

```
endmodule
```

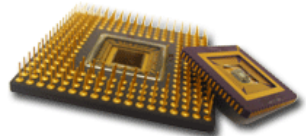



Edge-sensitive Timing Control (Even-Based)

Mat 2

Edge-sensitive (Even-based) timing controls: **@(<signal>)**


- Delays execution until an **edge** occurs on signal.
- Syntax of <event>

@(<sensitivity>), for a single variable // always **@(a)**

@(<sensitivity_list>), for several variables // always **@(a or b or c)**


◆ A regular event is that signal <sensitivity> has

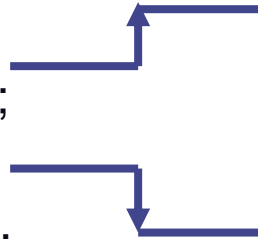- a change
 - ◆ E.g. **@(a) b = ~a;**
- a positive edge transition
 - ◆ E.g. **@(posedeg clk) q = d;**
- a negative edge transition
 - ◆ E.g. **@(negedge clk) q = d;**



Sensitivity List !!

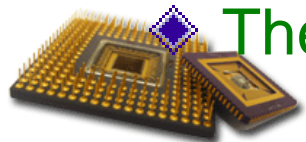◆ The keywords **posedge** and **negedge** will imply a **FF**.





Edge-sensitive Timing Control (Even-Based)

Mat 2

- ◆ Use the **@** timing control for combinational and sequential models at the RTL and behavioral levels.
- ◆ You can qualify signal sensitivity with the **negedge** and **posedge** keywords, and you can wait for changes on multiple signals by using the **or** keyword.

```
module reg_adder (out, a, b, clk);
```

```
    input clk;
```

```
    input [2:0]a,b;
```

```
    output [3:0]out;
```

```
    reg [3:0] out;
```

```
    reg [3:0] sum;
```

```
    always @(a or b) // When any change occurs on a or b
```

```
        #5 sum = a + b;
```

```
    always @(negedge clk) // at every negative edge of clk
```


```
        out = sum;
```

```
endmodule
```

Sensitivity List !!

Combinational block

Sequential block

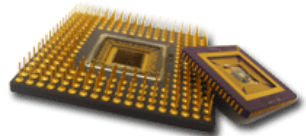



Edge-sensitive Timing Control Examples (1/2)



Mat 2

◆ Combinational circuit

- @ (a): act if signal 'a' changes.
 - ◆ Ex. always @ (a) $c \leq a + 1$;
- @ (a or b): act if signal 'a' or 'b' changes.
 - ◆ Ex. always @ (a or b) $c \leq a + b$;
- The sensitivity list **must** include all inputs

◆ Sequential circuit (Register)

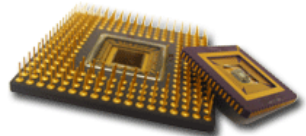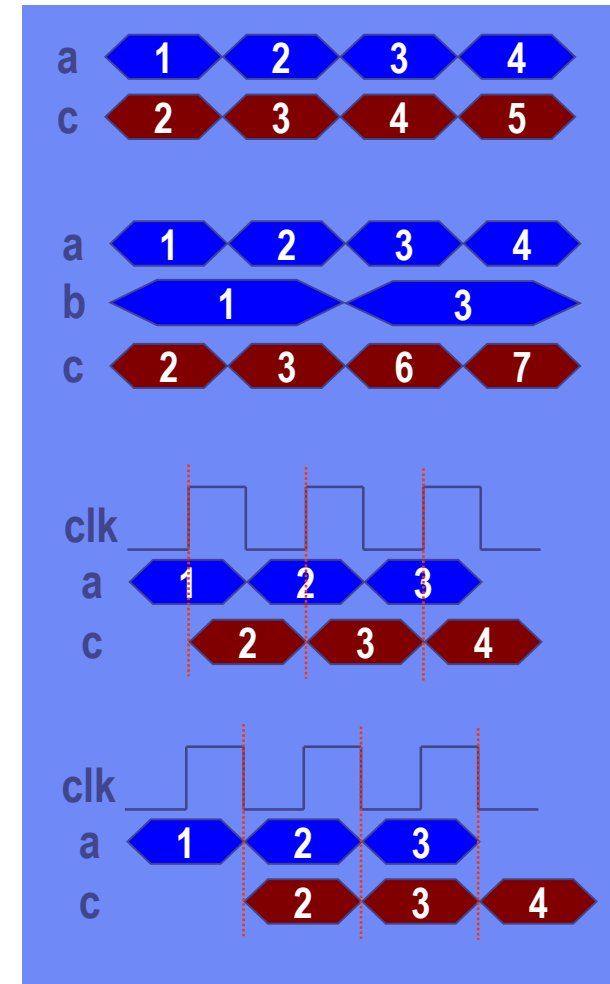- @ (posedge clk): act at the rising edge of clk signal.
 - ◆ Ex. always @ (posedge clk) $c \leq a + 1$;
- @ (negedge clk): act at the falling edge of clk signal.
 - ◆ Ex. always @ (negedge clk) $c \leq a + 1$;






Edge-sensitive Timing Control Examples (2/2)

Mat 2

Register Inference


```
module Comb (A, B, C, Y);  
  input A, B, C;  
  output Y;  
  reg Y;
```

```
  always @ (A or B or C)  
  begin  
    Y = A | B | C;  
  end  
endmodule
```

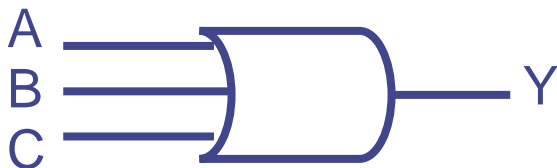

```
module SEQ (CLK, A, B, C, Y);  
  input CLK, A, B, C;  
  output Y;  
  reg Y;
```

```
  always @ (posedge CLK)  
  begin  
    Y = A | B | C;  
  end  
endmodule
```

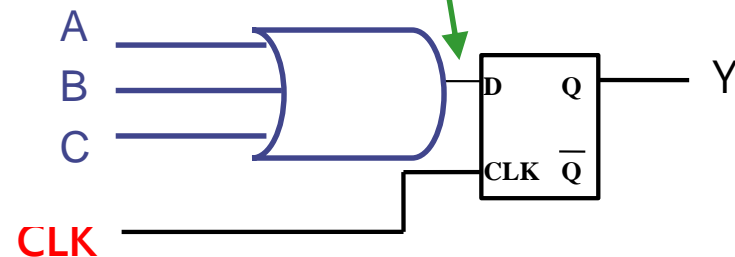

所以，宣告reg，並不一定會合成一個hardware register



Components in Procedural Blocks

Mat 2

◆ Procedural blocks have the following components:

控制電路何時/
何種條件動作

描述電
路行為

- Timing controls to control the execution of the block and the statements in the block
- Procedural assignment statements to describe the data flow *within the block*
- High-level constructs (loops, conditional statements) to describe the functional operation of the block

Procedural block

```
module add_mul(out, a, b);
input [2:0] a, b;
output [3:0] out;
reg [3:0] out;
```

Timing control


```
always@(a or b)
if (a > b)
out = #5 a + b;
```

```
else
out = #8 a * b;
```

High level
constructs

Procedural
assign

```
endmodule
```

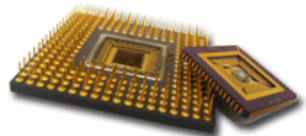



Procedural Assignments

Mat 2


- ◆ Assignments made inside **procedural blocks** are called **procedural assignments**.
- ◆ All signals on the **left**-hand side must be a **register data type** (such as type **reg**).
- ◆ The **right**-hand side of a procedural assignment can be any valid expression. The data types used here are **not restricted**.
- ◆ If you forget to declare a signal, it defaults to type **wire**. If you make a procedural assignment to a **wire**, it is an **ERROR**.

```
module adder (out, a, b, cin);
input a, b, cin;
output [1:0] out;
wire a, b, cin;
reg sum;
reg [1:0] out;
```

```
always @(a or b or cin)
```

```
begin
sum = a ^ b ^ cin ; // OK
carry = a & b | b & cin | a & cin ;
           // ERROR! (必須宣告為reg)
           // carry is not declared,
           // and defaults to a 1-bit wire.
out = {carry, sum} ;
end
endmodule
```

Procedural Assignments

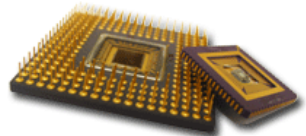



Procedural Assignments

Mat 2

◆ The Verilog HDL contains **two** types of procedural assignment


- **Blocking** procedural assignment //循序式的方式執行程式
- **Non-blocking** procedural assignment //平行式的方式執行程式

Blocking :

```
a = 0;  
b = 0;
```

Non-blocking :

```
a <= 0;  
b <= 0;
```

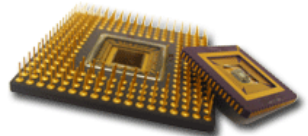




Blocking vs. Nonblocking

Mat 2

- ◆ A blocking procedural assignment is **executed (assign) before** the next statement in the sequential block is **scheduled (read)**.
- ◆ A nonblocking assignment does not block the procedural flow, so as soon as the assignment is read by the simulator and scheduled, the next assignment can be read. Then, they are assigned (execute) concurrently.
 - When all assignments in a procedural block are nonblocking, the assignments happen in two steps:
 1. The simulator evaluates all the RHS expressions, stores the resulting values, and schedules the assignments to take place at the time specified by timing control.
 2. After each delay has expired, the simulator executes the assignment by assigning the stored values to the LHS expression.

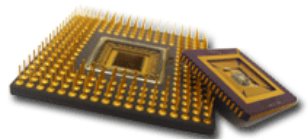



Examples (1/3)

Mat 2


```

module non_block1;
  reg a, b, c, d, e, f;
  initial begin //blocking assignments
    a = #10 1; // time 10
    b = #2 0;  // time 12
    c = #4 1;  // time 16
  end
  initial begin //non-blocking assignments
    d <= #10 1; // time 10
    e <= #2 0 ; // time 2
    f <= #4 1 ; // time 4
  end
  initial begin
    $monitor($time,,"a= %b b= %b c= %b d= %b e= %b f= %b", a, b, c, d, e, f);
    #100 $finish;
  end
endmodule

```

◆ The simulation result :

0	a=x	b=x	c=x	d=x	e=x	f=x
2	a=x	b=x	c=x	d=x	e=0	f=x
4	a=x	b=x	c=x	d=x	e=0	f=1
10	a=1	b=x	c=x	d=1	e=0	f=1
12	a=1	b=0	c=x	d=1	e=0	f=1
16	a=1	b=0	c=1	d=1	e=0	f=1

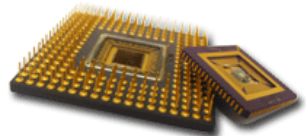




Examples (2/3)

Mat 2

```
module swap_vals;
  reg a, b, clk;
  initial
    begin
      a = 0;
      b = 1;
      clk = 0;
    end
  always #5 clk = ~clk;
  always @(posedge clk)
    begin
      a = b; // a = 1
      b = a; // b = a = 1
    end
endmodule
```

```
always @(posedge clk)
  begin
    a <= b; // a = 1
    b <= a; // b = 0
  end
```

◆ **swaps** the values of a and b.

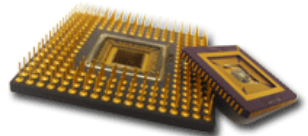



Examples (3/3)

Mat 2

◆ Blocking assignment



always @(posedge clk) **i.e. $a = b = c$**

begin

$b = a;$

$c = b;$

end

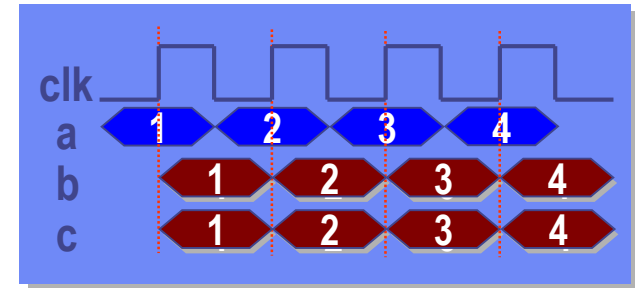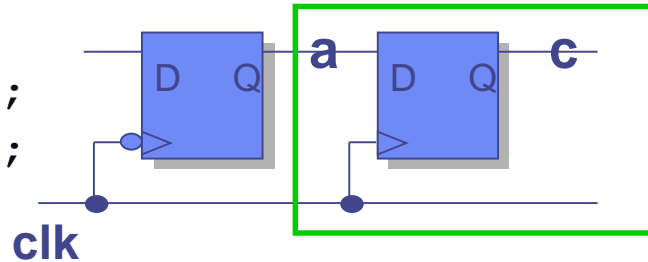

◆ Nonblocking assignment




always @(posedge clk)

begin

$b <= a;$

$c <= b;$

end

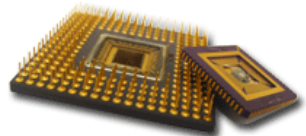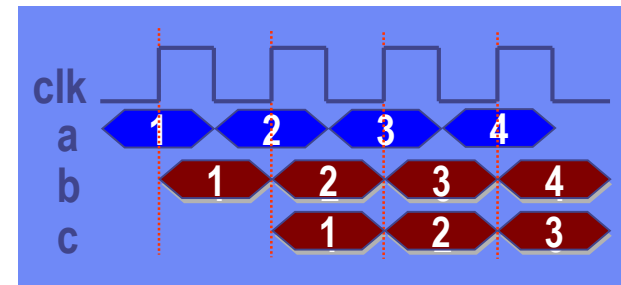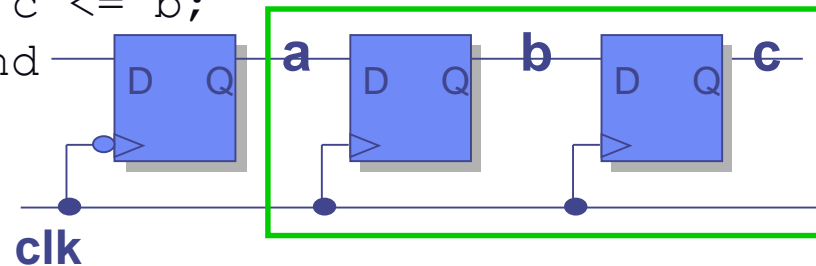




Coding Style for Synthesis (1/2)

Mat 2

- ◆ Use non-blocking assignments within sequential always block.
- ◆ Example:


```
always @(posedge clock) begin
    x <= a;
    y <= x;
    z <= y;
end
```

Usually you expect

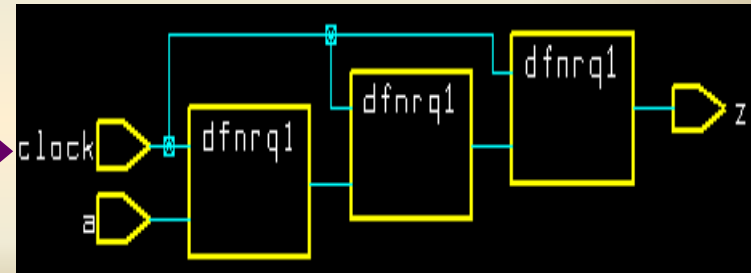

```
always @(posedge clock) begin
    x = a;
    y = x;
    z = y;
end
```

May not you expect

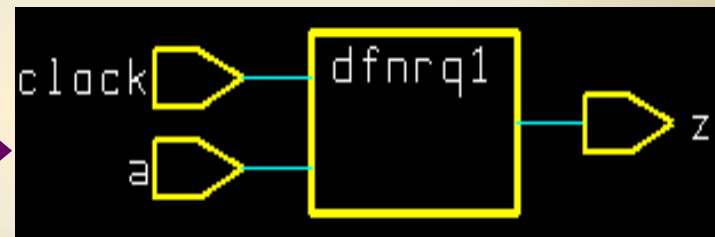




Coding Style for Synthesis (2/2)

Mat 2

- ◆ Use blocking assignments within combinational always block.
- ◆ Example:


```
always @(a or b or x) begin
    x = a & b;
    y = x | b;
    x = a;
end
```

Usually you expect

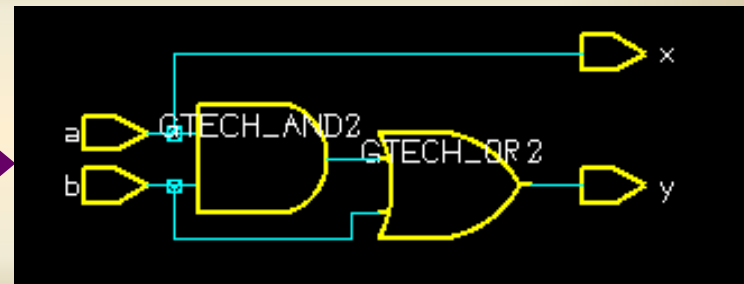

```
always @(a or b or x) begin
    x <= a & b;
    y <= x | b;
    x <= a;
end
```

May not you expect

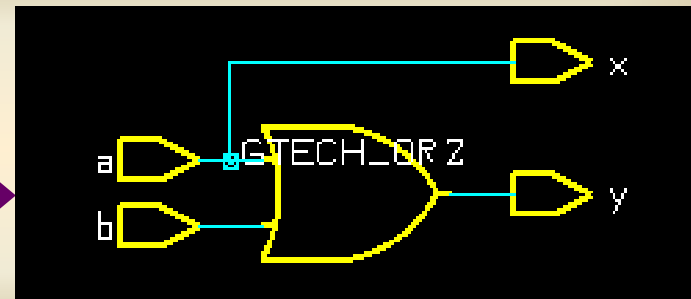



Components in Procedural Blocks

Mat 2

◆ Procedural blocks have the following components:

控制電路何時/
何種條件動作

描述電
路行為

- Timing controls to control the execution of the block and the statements in the block
- Procedural assignment statements to describe the data flow within the block
- High-level constructs (loops, conditional statements) to describe the functional operation of the block

Procedural block

```
module add_mul(out, a, b);
input [2:0] a, b;
output [3:0] out;
reg [3:0] out;
```

Timing control

```
always@(a or b)
```

```
if (a > b)
```

```
out = #5 a + b;
```


```
else
```

```
out = #8 a * b;
```

High level
constructs

Procedural
assign

```
endmodule
```

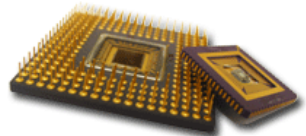




Behavioral Control Statements

◆ Conditional Statements

- **If; If-else**
- **case**

◆ Looping Statements

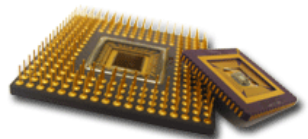- **forever loop**
- **repeat loop**
- **while loop**
- **for loop**






Conditional Statements: *if* (1/4)

Mat 2

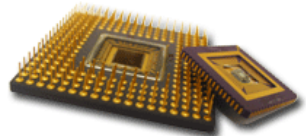- ◆ If true (1), the true_statement is executed. If **false (0)** or **ambiguous (x)**, the false_statement is executed
- ◆ To ensure proper readability and proper association, use ***begin...end*** block statements.
- ◆ Types of Conditional Statements
 - **Type 1**: no else statement
 - **Type 2**: one else statement
 - **Type 3**: nested if-else-if statement






Conditional Statements: *if* (2/4)

Mat 2

Type 1: no else statement

Syntax:



if *<condition_expression>* *<statement>*

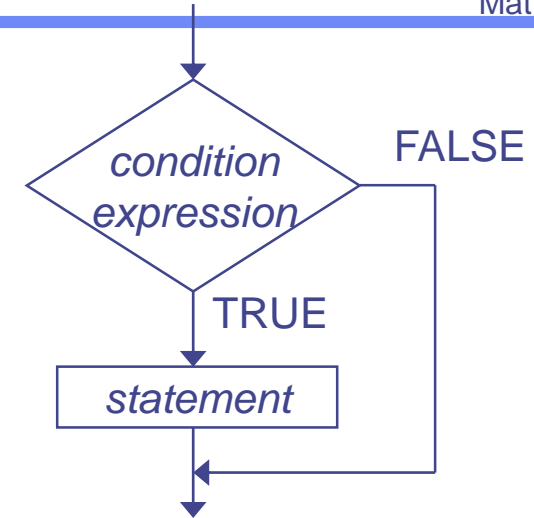

Type 2: one else statement

Syntax:

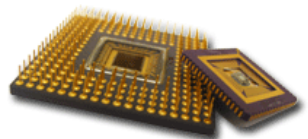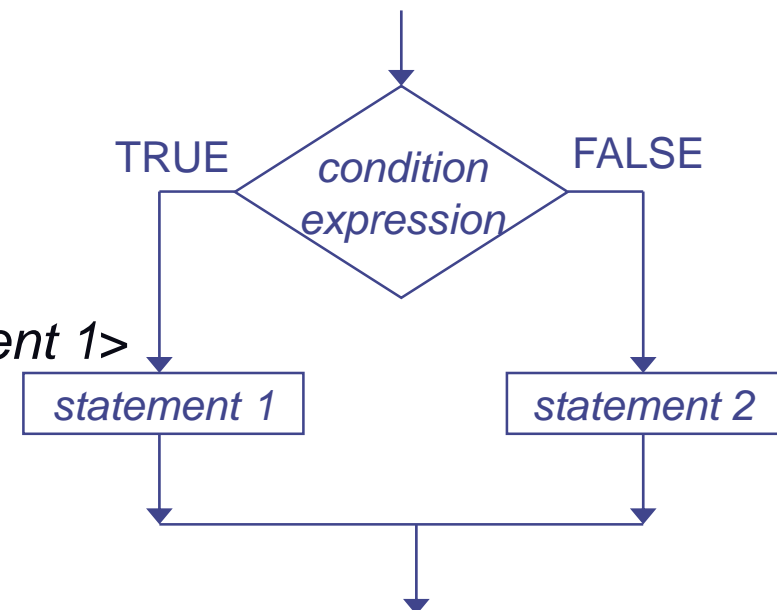if *<condition_expression>* *<statement 1>*
else *<statement 2>*





Conditional Statements: *if* (3/4)

Mat 2

Example

```
always #20
```

```
if (index > 0) // Beginning of outer if
```

```
    if (rega > regb) // Beginning of the 1st inner if  
        result = rega;
```

```
    else
```

```
        result = 0; // End of the 1st inner if
```

```
else
```

```
    if (index == 0)
```

```
        begin
```


```
            $display("Note : Index is zero");
```

```
            result = regb;
```

```
        end
```

```
    else
```
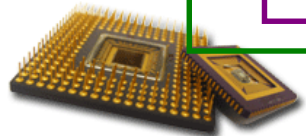
```
        $display("Note : Index is negative");
```





Conditional Statements: *if* (4/4)

Mat 2

Type 3: nested if-else-if statement



Syntax:

```

if <condition_expression1> <statement1>
else if <condition_expression2> <statement2>
.....
else if <condition_expressionN> <statementN>
else <default_statement>
  
```

- ◆ The expressions are evaluated in order; if any expression is true, the statement associated with it is executed, and this terminates the whole chain.
- ◆ Each statement is either a single statement or a block (**begin...end**) statements.
- ◆ The last else part of the if-else-if construct handles the default case where none of the other conditions was satisfied.

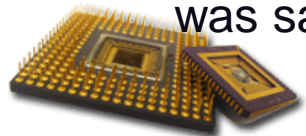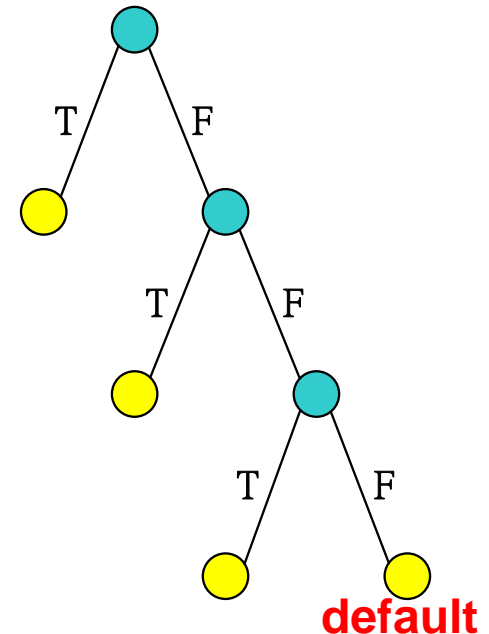always
 if (index < stage1)
 result = a + b;
 else if (index < stage2)
 result = a – b;
 else
 result = a;






Conditional Statements: *case* (1/4)

Mat 2

- ◆ The **case** statement is a special **multiway** conditional statement that tests whether the expression matches one of a number of other expressions and branches accordingly.
 - The **case** statement does a bit-by-bit comparison for an **exact match** (including x and z)
 - The **default** statement is optional. It is executed when none of the statements match the case expression. If it is not specified, Verilog takes no action.
 - Use of **multiple default** statements is illegal.
- ◆ It is a good programming practice to always use the **default** statement, especially to check for x and z (**To avoid synthesis tool to produce Latch device**).

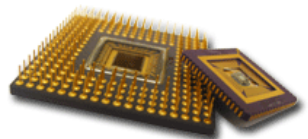




Conditional Statements: *case* (2/4)

Mat 2

Syntax
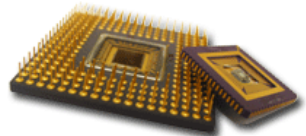
```
case (<expression>)  
    <alternative 1> : <statement 1>  
    <alternative 2> : <statement 2>  
    .....  
    <alternative N> : <statement N>  
    default : <default_statement>  
endcase
```





Conditional Statements: *case* (3/4)

Mat 2

- ◆ **case** is easier to read than a long string of **if...else** statements

```
module mux_2_to_1(a, b, out, sel);  
  input a, b, sel;  
  output out;  
  reg out;
```

```
  always @ (a or b or sel)  
  begin
```

```
    if (sel) out = a;  
    else out = b;
```

```
  end
```

```
endmodule
```


=

```
case (sel)
```

```
  1'b1: out = a;
```

```
  1'b0: out = b;
```

```
endcase
```

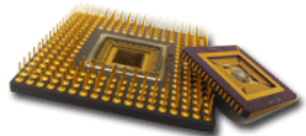




Conditional Statements: *case* (4/4)

Mat 2

```
module compute (result, rega, regb, opcode);  
    input [7:0] rega, regb;  
    input [2:0] opcode;  
    output [7:0] result;  
    reg [7:0] result;  
    always @(rega or regb or opcode)
```

```
        case (opcode)  
            3'b000 : result = rega + regb;  
            3'b001 : result = rega - regb;  
            ...  
            3'b010 : result = rega * regb;  
            3'b100 : result = rega / regb;  
            default : begin  
                result = 8'b0;  
                $display ("no match");  
            end  
        endcase
```

```
    endmodule
```

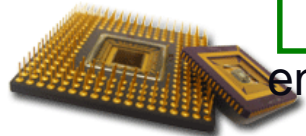




Behavioral Control Statements

◆ Conditional Statements

- If; if-else
- case

◆ Looping Statements

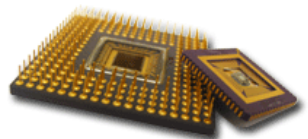- forever loop
- repeat loop
- while loop
- for loop






Looping Statements

Mat 2

- ◆ There are **four** types of looping statements. They provide a means of controlling the execution of a statement zero, one, or more times.
 - **forever** continuously executes a statement.
 - **repeat** executes a statement a fixed number of times.
 - **while** executes a statement until an expression becomes false. If the expression starts out false, the statement is not executed at all.
 - **for** controls execution of its associated statement by a three-step process, as follows :
 1. initialize a variable
 2. evaluates an expression
 3. modify the value of the loop-control variable

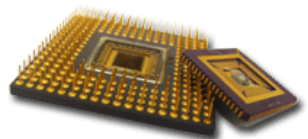




Looping Statements: *forever*

Mat 2

- ◆ The following style of behavioral clock is very flexible (you can control the start time and duty cycle) and simulates very efficiently.
- ◆ A **forever** loop executes a statement (or block of statements) **until the simulation ends**.
- ◆ A **forever** loop should be the last item in a procedural **begin/end** block, as any statement that followed it would never be executed.
- ◆ **forever** loops are **not synthesizable**. They are generally implemented in **test benches** only.
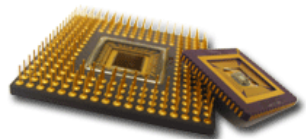
```
...  
reg clk;  
initial  
begin  
    clk = 0;  
    forever  
        begin  
            #10 clk = 1;  
            #10 clk = 0;  
        end  
    end  
end  
...
```





Looping Statements: *repeat*

Mat 2

- ◆ A **repeat** loop executes a block of statements a **fixed number** of times.
- ◆ The value of loop count variable is determined once at the beginning of the execution of the loop. It's not possible to exit loop by changing the loop count variable. (see EX2)
- ◆ The **repeat** is **not efficient** for **synthesis**, it could be used in **testbench** modules only.

Ex1:

```

parameter wordlength = 16;
reg CRC_valid;
initial begin
    repeat ( wordlength-1) begin
        CRC_valid = check ^ datai;
    end
end

```


Ex2:

```

initial begin
    count = 0;
    NUM = 10;
    #30 NUM = 30;
end
initial begin
    repeat (NUM) begin
        #10 count = count+1; // count = 10
    end
end

```

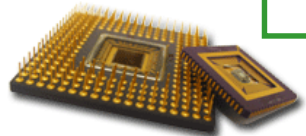→ Changing loop count variable can not interrupt the repeat loops





Looping Statements: *while*

Mat 2

- ◆ A **while** loop executes a statement (or block of statements) as long as its expression is **true** (or nonzero).
- ◆ If the expression is initially false, the statements are not executed.
- ◆ The **while** loop is **not efficient** for **synthesis**, it could be used in **testbench** modules only.


```

reg [7:0] tempreg;
reg [3:0] count;
...
count = 0;
while (tempreg) // Count the ones in tempreg
begin
    if (tempreg[0]) count = count + 1;
    tempreg = tempreg >> 1; // Shift right
end

```

...

tempreg	count
101	1
010	1
001	2

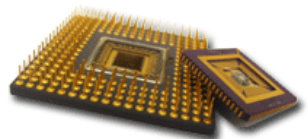



Looping Statements: *for*

Mat 2

◆ **Syntax:** `for (<initialization>; <condition>; <operation>)`

1. The **initialization** is performed on the loop index.
2. The loop executes as long as the **condition** evaluates to TRUE.
3. After each time the loop executes, the **operation** is performed.

◆ A simple comparison to zero often suffices in a **for** loop, and is usually handled much faster. However, this type of comparison may not be accepted by your synthesis tool.

// X detection


```
for (index = 0; index < size; index = index + 1)
    if (val[index] == 1'bx)
        $display ("found an X");
```

// Memory load; " $\neq 0$ " is simulated efficiently

```
for (i = size; i  $\neq$  0; i = i - 1)
    memory[i-1] = 0;
```

// Factorial sequence
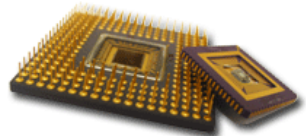
```
factorial = 1;
for (j = num; j  $\neq$  0; j = j - 1)
    factorial = factorial * j;
```






Put Things at the Right Place

Mat 2

```
module adder (...);  
  
always @(...)  
begin  
    and (a, b, c );  
    assign sum = a + b;  
end  
  
endmodule
```

```
module adder (...);  
  
sum = a + b ;  
  
always @(...)  
begin  
    ....  
end  
  
endmodule
```
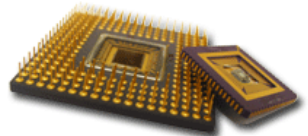
```
module adder (...);  
  
If (sl==1);  
    sum = a+b;  
  
always @(...)  
begin  
    ....  
end  
  
endmodule
```





References

Mat 2

- ◆ Cadencd, “Verilog-XL Reference”, Product version 3.1, August 2000.
- ◆ Synopsys, “HDL Compiler for Verilog: Reference Manual”, Version 1999.05, May 1999.
- ◆ Samir Palnitkar, “Verilog HDL: A Guide to Digital Design and Synthesis”, Prentice Hall.
- ◆ Michael D.Ciletti, “Advanced Digital Design with the VERILOG HDL”, Prentice Hall.
- ◆ 教育部「超大型積體電路與系統設計」教育改進計畫課程資料
- ◆ 黃俊銘, “Cell-Based IC Design Concepts”, CIC訓練課程
- ◆ 王旭昇, “Logic Synthesis with Design Compiler”, CIC訓練課程
- ◆ Verilog教學網站

